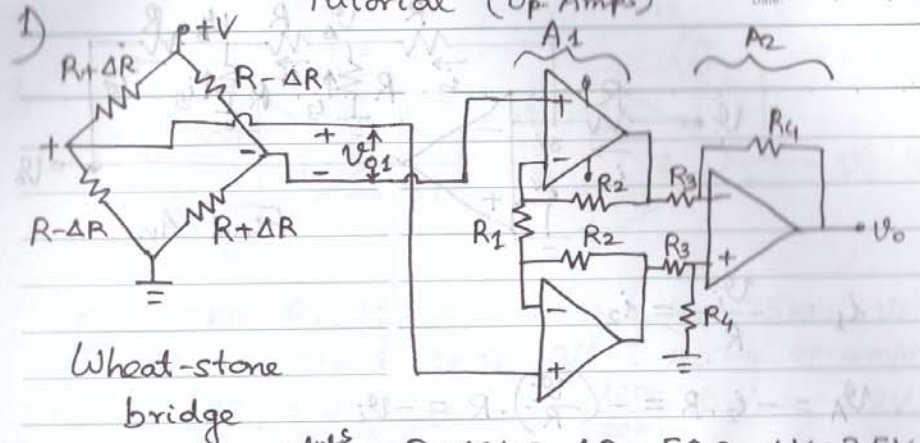


No.

Date.

Tutorial (Op-Amps)

Wheat-stone
bridge→ Calc. values
of R

$$R = 10\text{ k}\Omega, \Delta R = 50\text{ }\Omega, +V = 3.5\text{ V}$$

Design an amp. for $V_o = 5\text{ V}$ when $\Delta R = 50\text{ }\Omega$

$$\begin{aligned} \text{Sol}^n: V_{o1} &= \left[\frac{R - \Delta R}{(R - \Delta R) + (R + \Delta R)} - \frac{R + \Delta R}{(R + \Delta R) + (R - \Delta R)} \right] \cdot V \\ &= \left[\frac{R - \Delta R}{2R} - \frac{R + \Delta R}{2R} \right] \cdot V \\ &= -\frac{\Delta R}{R} \cdot (+V) = -\frac{50}{10 \times 10^3} (3.5) = -1.75 \times 10^{-3} \\ &= 17.5\text{ mV} \end{aligned}$$

$$\text{Required gain} = A_d = \frac{V_o}{V_i} = \frac{5}{17.5\text{ m}} = 285.714$$

For an instrumentation amp.,

$$|A_d| = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) = 285.714$$


$$\text{Assume, } R_3 = 10\text{ k}\Omega \text{ \& } R_4 = 150\text{ k}\Omega$$

$$\therefore \frac{R_2}{R_1} = 9.02$$

$$\text{Let, } R_2 = 100\text{ k}\Omega, \therefore R_1 = 11.1\text{ k}\Omega$$

(Ans)

2.

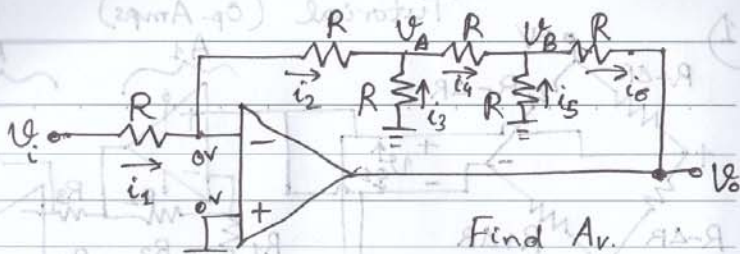

Find A_v .

$$i_1 = \frac{V_i}{R} = i_2$$

$$V_A = -i_2 \cdot R = -\left(\frac{V_i}{R}\right) \cdot R = -V_i$$

$$i_3 = -\frac{V_A}{R} = -\frac{-V_i}{R} = \frac{V_i}{R}$$

$$i_4 = i_2 + i_3 = -\frac{V_A}{R} - \frac{V_A}{R} = -\frac{2V_A}{R} = +\frac{2V_i}{R}$$

$$V_B = V_A - i_4 \cdot R = -V_i - \left[+\frac{2V_i}{R}\right] \cdot R = -3V_i$$


$$i_5 = -\frac{V_B}{R} = -\frac{-3V_i}{R} = \frac{3V_i}{R}$$

$$i_6 = i_4 + i_5 = \frac{2V_i}{R} + \frac{3V_i}{R} = \frac{5V_i}{R}$$

$$V_o = V_B - i_6 \cdot R = -3V_i - \left(\frac{5V_i}{R}\right) \cdot R = -8V_i$$

$$\Rightarrow \frac{V_o}{V_i} = A_v = -8 \quad (\text{Ans})$$

3.

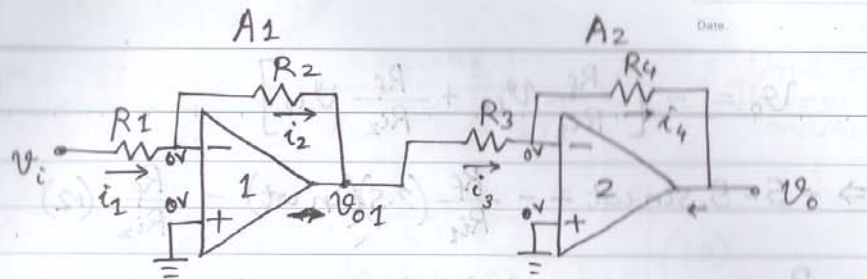

$$R_1 = 20k\Omega, R_2 = 120k\Omega, R_3 = 15k\Omega, R_4 = 75k\Omega, V_i = 0.2V$$

Find: V_{o1}, V_o, i_1 to i_4 , O/P I in the op-amps.

$$\text{Sol}^n \quad V_{o1} = -\frac{R_2}{R_1} \cdot V_i = -\frac{120k}{20k} \cdot (0.2) = -1.2V \quad (\text{Ans})$$

$$V_o = -\frac{R_4}{R_3} \cdot V_{o1} = -\frac{75k}{15k} \cdot (-1.2) = +6V \quad (\text{Ans})$$


$$i_1 = i_2 = \frac{0.2}{20k} = 10\mu A \quad (\text{Ans})$$

$$i_3 = i_4 = \frac{V_{o1}}{R_3} = \frac{-1.2}{15k} = -80\mu A \quad (\text{Ans})$$

$$\left. \begin{array}{l} \text{O/P I (op-amp.1)} = -(10\mu + 80\mu) = -90\mu A \\ \text{O/P I (op-amp.2)} = +80\mu A \end{array} \right\} \begin{array}{l} \text{Sink I} \\ \text{Source I} \end{array} \quad (\text{Ans})$$

4. Design a Summing amp: $V_{i1} = (2.5)\sin\omega t$ (V), $V_{i2} = +2V$, $V_o = -5(1 + \sin\omega t)$ (V). Largest R is $200k\Omega$.

Solⁿ.

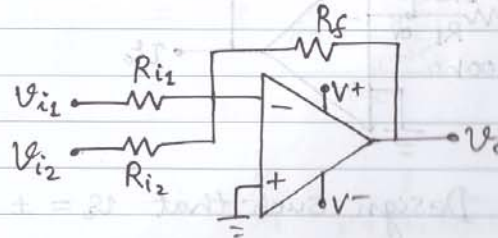

$$V_o = - \left[\frac{R_f}{R_{i1}} V_{i1} + \frac{R_f}{R_{i2}} V_{i2} \right]$$

$$\Rightarrow -5 = 5 \sin \omega t = - \frac{R_f}{R_{i1}} (2.5 \sin \omega t) - \frac{R_f}{R_{i2}} (2)$$

By separating LHS & RHS elements,

$$-5 = - \frac{R_f}{R_{i2}} \cdot 2$$

$$\Rightarrow \frac{R_f}{R_{i2}} = 2.5$$

Indicates $\Rightarrow R_f > R_{i2}$


$$\therefore R_f = 200 \text{ k}\Omega \quad (\text{largest } R \text{ in the ckt})$$

Now,

$$-5 (\sin \omega t) = - \frac{200 \text{ k}}{R_{i1}} (2.5 \sin \omega t)$$

$$\Rightarrow R_{i1} = \frac{200 \text{ k} \cdot (2.5)}{5} = 100 \text{ k}\Omega \quad (\text{Ans})$$
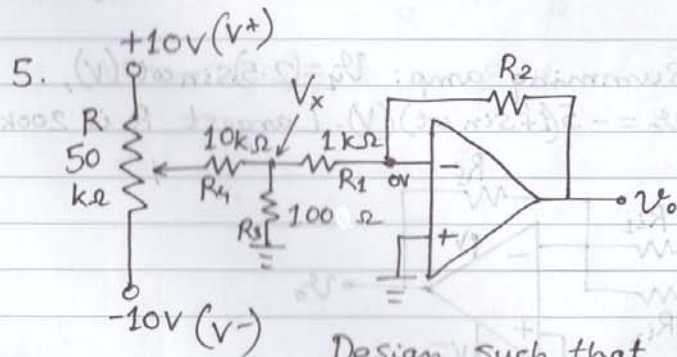
$$\text{Also, } R_{i2} = \frac{R_f}{2.5} = \frac{200 \text{ k}}{2.5} = 80 \text{ k}\Omega \quad (\text{Ans})$$



Design such that $V_o = \pm 10 \text{ V}$.

Solⁿ. $V_{x(\max)} = \frac{R_3 // R_4}{R_3 // (R_1 + R_4)} \cdot V^+$ (Under Thevenin's condition)

$$= \frac{(0.1)(1)}{0.1+1} \cdot (10)$$


$$= \frac{(0.1)(1+10)}{0.1+1+10}$$

$$= 0.090 \text{ V}$$

Now, $|V_o| = \frac{R_2}{R_1} \cdot V_{x(\max)}$

$$\Rightarrow 10 = \frac{R_2}{1 \text{ k}} (0.090)$$
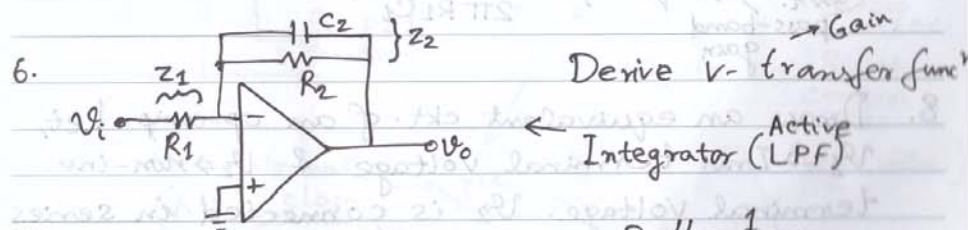
$$\Rightarrow R_2 = 111 \text{ k}\Omega \quad (\text{Ans})$$




Solⁿ. $A_v = \frac{V_o}{V_i} = - \frac{Z_2}{Z_1} = - \frac{R_2 // \frac{1}{j\omega C_2}}{R_1}$

$$= - \frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}}$$

$$= - \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_2}$$

$$= - \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_2} \quad (\text{Ans})$$

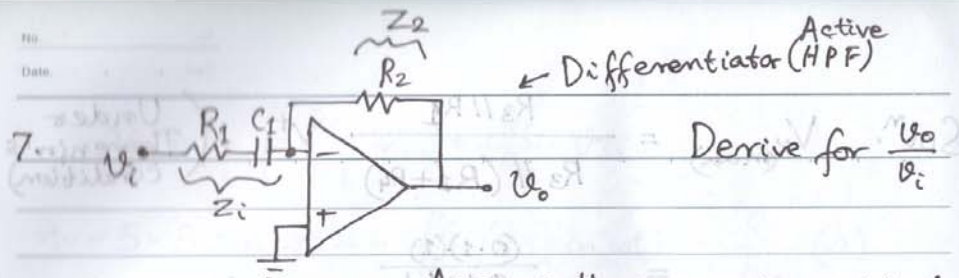Corner
(-3 db) freq. = $f_c = \frac{1}{2\pi R_2 C_2}$
w.r.t. pass-band gain



Solⁿ. Assume the op-amp is an ideal one.

$$\frac{V_o}{V_i} = - \frac{Z_2}{Z_1} = - \frac{R_2}{R_1 + \frac{1}{j\omega C_1}}$$


$$= - \frac{R_2 (j\omega C_1)}{1 + j\omega R_1 C_1}$$

$$= - \frac{R_2}{R_1} \cdot \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} \quad (\text{Ans})$$

Corner
(-3 db) freq.
w.r.t.
pass-band
gain


$$f_c = \frac{1}{2\pi R_1 C_1}$$

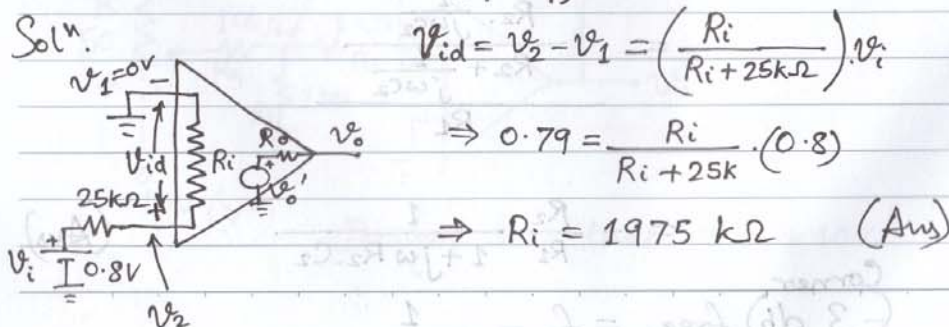8. Draw an equivalent ckt. of an op-amp. Let, $V_1 \Rightarrow$ Inv. terminal voltage & $V_2 \Rightarrow$ non-inv. terminal voltage. V_2 is connected in series with a $25\text{ k}\Omega$ resistor from a source of 0.8 V & $V_1 = 0\text{ V}$. What is $R_{i\min}$ such that $V_{id} = 0.79\text{ V}$? (op-amp)



No. _____ Date _____

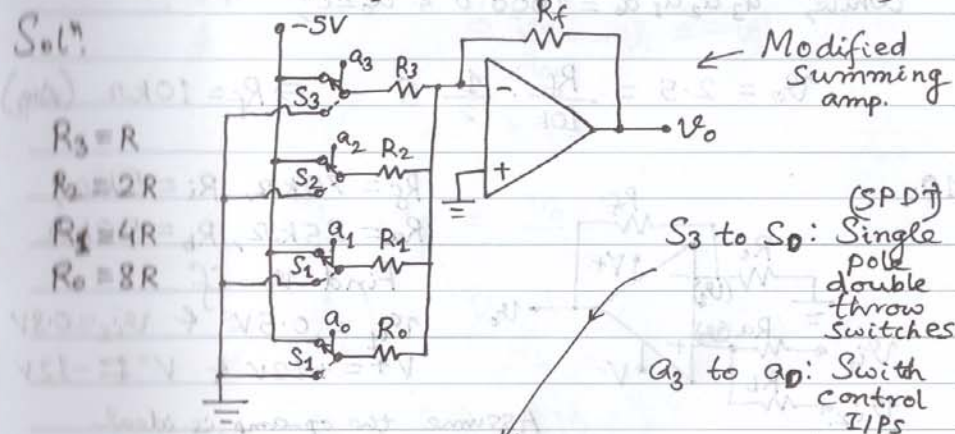9. Draw the circuit of a digital-to-analog converter (DAC) by using op-amp. Write the expression for its O/P voltage as a function of digital logic. Find the feedback resistor's value such that $V_o = +2.5\text{ V}$ while digital I/Ps are: $a_3 a_2 a_1 a_0 = 1000$, where, a_3 is the most significant bit, & a_0 is the least significant bit. (MSB) (LSB)



(Logic values)

Normally closed terminal (NC) → Pole terminal (P)
Normally open terminal (NO) → Switch control I/Ps

When, $a_n = '0' \Rightarrow 'P'$ is connected to 'NC'
" $a_n = '1' \Rightarrow 'P'$ " " " 'NO'

$$V_o = - \frac{R_f}{R_3} \cdot a_3 \cdot (-5) - \frac{R_f}{R_2} \cdot a_2 \cdot (-5) - \frac{R_f}{R_1} \cdot a_1 \cdot (-5) - \frac{R_f}{R_0} \cdot a_0 \cdot (-5)$$

$$= \frac{R_f}{R} \cdot a_3(5) + \frac{R_f}{2R} \cdot a_2(5) + \frac{R_f}{4R} \cdot a_1(5) + \frac{R_f}{8R} \cdot a_0(5)$$

Let, $R = 20k\Omega$.


$$\therefore V_o = \frac{R_f}{20k} \cdot a_3 \cdot 5 + \frac{R_f}{40k} \cdot a_2 \cdot 5 + \frac{R_f}{80k} \cdot a_1 \cdot 5 + \frac{R_f}{160k} \cdot a_0 \cdot 5$$

$$\therefore V_o = \frac{R_f}{10k} \left[\frac{a_3}{2} + \frac{a_2}{4} + \frac{a_1}{8} + \frac{a_0}{16} \right] (5) \quad (\text{Ans})$$

While, $a_3 = 1, a_2 = 0, a_1 = 0$ & $a_0 = 0$;

$$V_o = 2.5 = \frac{R_f}{10k} \cdot \frac{1}{2} \cdot 5 \Rightarrow R_f = 10k\Omega \quad (\text{Ans})$$

10.

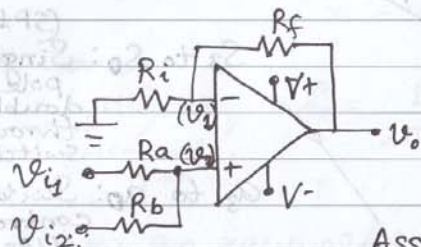

$R_f = 70k\Omega, R_i = 5k\Omega,$
 $R_a = 25k\Omega, R_b = 50k\Omega$
Find V_o if
 $V_{i1} = 0.5V$ & $V_{i2} = 0.8V$
 $V^+ = +12V$ & $V^- = -12V$

Assume the op-amp is ideal.

Solⁿ. Apply superposition:

$$\text{For, } V_{i2} = 0V, V_2 = \frac{R_b}{R_a + R_b} V_{i1} = \frac{50k}{25k + 50k} \cdot V_{i1}$$

$$V_o(V_{i1}) = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{R_b}{R_a + R_b}\right) V_{i1}$$

$$= \left(1 + \frac{70k}{5k}\right) \left(\frac{50k}{25k + 75k}\right) V_{i1} = 10 V_{i1}$$

$$\text{For, } V_{i1} = 0V, V_2 = \frac{R_a}{R_a + R_b} V_{i2}$$

$$V_o(V_{i2}) = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{R_a}{R_a + R_b}\right) V_{i2} = 5 V_{i2}$$


$$V_o = V_o(V_{i1}) + V_o(V_{i2})$$

$$= 10 V_{i1} + 5 V_{i2} \checkmark$$

$$= 10(0.5) + 5(0.8) = 9V \quad (\text{Ans})$$

11. Derive the eqⁿ of the gain of a practical non-inv. amp. using an op-amp.

Solⁿ.

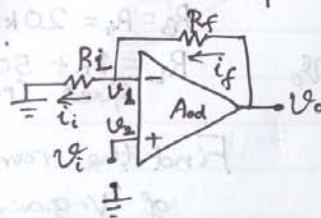

$$V_o = A_{od}(V_2 - V_1)$$

$$\Rightarrow V_o = A_{od}(V_i - V_1)$$

$$\Rightarrow \frac{V_o}{A_{od}} - V_i = -V_1$$

$$\text{or, } V_1 = V_i - \frac{V_o}{A_{od}}$$

Now,

$$i_i = \frac{V_1}{R_i} = i_f = \frac{V_o - V_i}{R_f}$$

$$\therefore V_1 \left(\frac{1}{R_i}\right) = \frac{V_o - V_i}{R_f}$$

$$\Rightarrow V_1 \left(\frac{1}{R_i} + \frac{1}{R_f}\right) = \frac{V_o}{R_f}$$

$$\Rightarrow V_o \left(1 + \frac{R_f}{R_i}\right) V_1 = \left(1 + \frac{R_f}{R_i}\right) \left(V_i - \frac{V_o}{A_{od}}\right)$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{\left(1 + \frac{R_f}{R_i}\right)}{1 + \frac{1}{A_{od}} \left(1 + \frac{R_f}{R_i}\right)} \quad (\text{Ans})$$