

$$i_i = \frac{O - V_i}{R_i} = \frac{V_i - V_o}{R_f}$$


$$\Rightarrow V_o = + \left( 1 + \frac{R_f}{R_i} \right) V_i$$

$$\text{Gain (A}_v\text{)} = + \left( 1 + \frac{R_f}{R_i} \right)$$


$0^\circ$  phase shift

I/P resistance ( $R_i$ ) =  $\infty$  (or  $G \rightarrow 0$ )

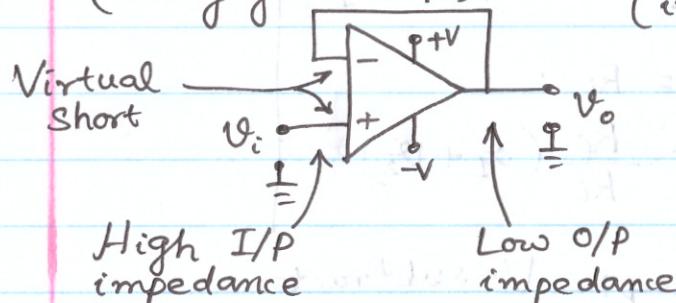→ Voltage follower: Special case of a non-inv. amp.  
(Unity-gain amp.) (impedance converter)





$$A_v = \frac{V_o}{V_i} = 1$$

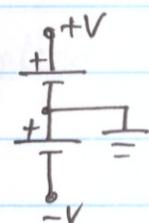

$$V_o = \left( 1 + \frac{R_f}{R_i} \right) V_i = \left( 1 + \frac{0}{\infty} \right) V_i = V_i$$

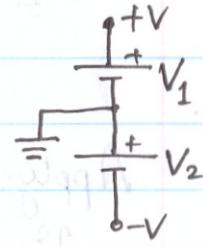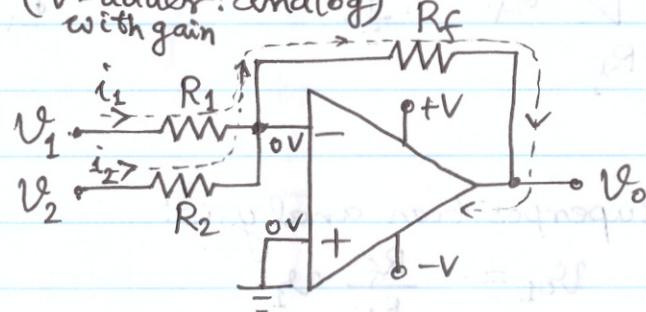iii) Summing amp: Special case of an inv. amp.  
(V-adder: analog with gain)



Analyze by using superposition system.

Assume,  $v_1$  is applied while  $v_2 = 0$

$$v_{o1} = -i_1 \cdot R_f = -\frac{R_f}{R_1} \cdot v_1$$

Assume,  $v_2$  is applied while  $v_1 = 0$

$$v_{o2} = -i_2 \cdot R_f = -\frac{R_f}{R_2} \cdot v_2$$

$$\therefore v_o = v_{o1} + v_{o2}$$


$$\Rightarrow v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2$$

$$\Rightarrow v_o = -\left[\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2\right]$$

If,  $R_1 = R_2 = R_i$ :

$$v_o = -\frac{R_f}{R_i} (v_1 + v_2)$$

IV) Difference amp: V-subtractor

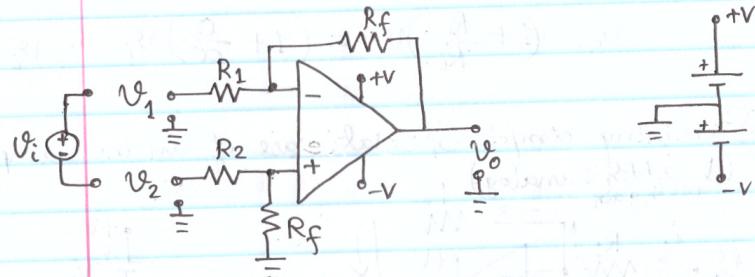

Applying superposition analysis:

$$v_2 = 0 : v_{o1} = -\frac{R_f}{R_1} v_1 \quad (\text{Inv. amp.})$$

$$v_1 = 0 : v_{o2} = \left[ \frac{R_f}{R_2 + R_f} \cdot v_2 \right] \left[ 1 + \frac{R_f}{R_1} \right] \quad (\text{Non-inv. amp.})$$

$$\Rightarrow v_{o2} = \left( 1 + \frac{R_f}{R_1} \right) \left[ \frac{\frac{R_f}{R_2}}{1 + \frac{R_f}{R_2}} \right] v_2$$

$$v_o = v_{o1} + v_{o2} = -\frac{R_f}{R_1} v_1 + \left( 1 + \frac{R_f}{R_1} \right) \left[ \frac{\frac{R_f}{R_2}}{1 + \frac{R_f}{R_2}} \right] v_2$$


$$\text{If, } R_1 = R_2 = R_i, \text{ or, } \frac{R_f}{R_1} = \frac{R_f}{R_2} = \frac{R_f}{R_i}$$

$$v_o = +\frac{R_f}{R_i} (v_2 - v_1)$$


Differential Gain

I/P resistance =  $2 \cdot R_i = R_I$

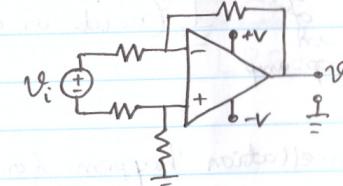Note: Differential I/P V may also be applied.



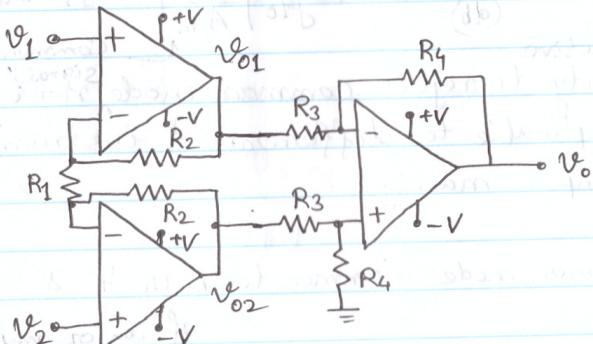
V) Instrumentation Amplifier: Special case of difference amp.



### Special Notes

1. Virtual ground/short:


i) Open loop analogy:

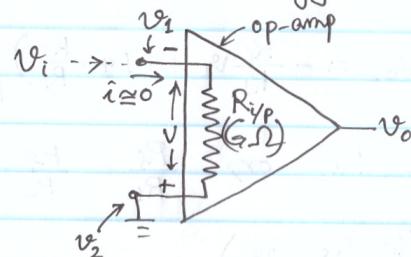

$$\text{If, } i=0, \quad R_{i/p} = G_\Omega$$

$$\begin{aligned} V &= V_2 - V_1 \\ &= i \cdot R_{i/p} \\ &= 0 \cdot (G_\Omega) \\ &= 0 \end{aligned}$$

ii) Closed loop analogy: Inv. amp.

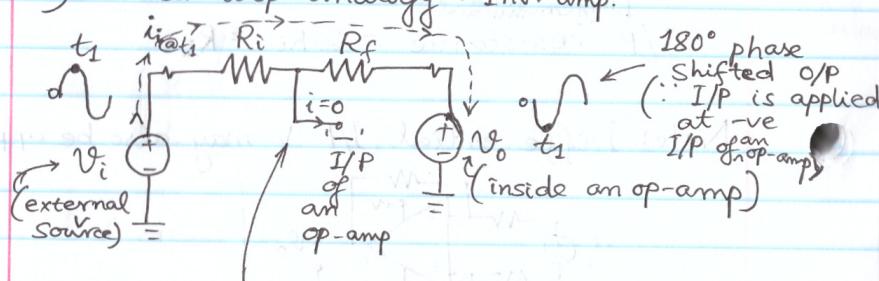

V-cancellation happens for  $V_i$  &  $V_o$

2. Common Mode Rejection Ratio (CMRR):


$$\text{CMRR (db)} = 20 \cdot \log_{10} \left| \frac{\text{Ad}}{\text{Acm}} \right|$$

Differential gain      Common-mode gain

Selective  
(Ability to reject common mode signal/noise)

Applicable to difference & instrumentation amps. mainly.

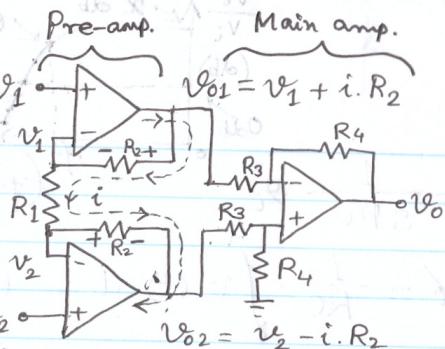Common mode: Common to both '+' & '-' inputs.  
of an op-amp/op-amp circuit




$$V_{o1} = V_1 + i \cdot R_2 = \left(1 + \frac{R_2}{R_1}\right) V_1 - \frac{R_2}{R_1} V_2$$

$$V_{o2} = V_2 - i \cdot R_2 = \left(1 + \frac{R_2}{R_1}\right) V_2 - \frac{R_2}{R_1} V_1$$


$$\text{Also, } V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1})$$

$$\Rightarrow V_o = \frac{R_4}{R_3} \underbrace{\left(1 + \frac{2R_2}{R_1}\right)}_{\text{Differential gain}} (V_2 - V_1)$$

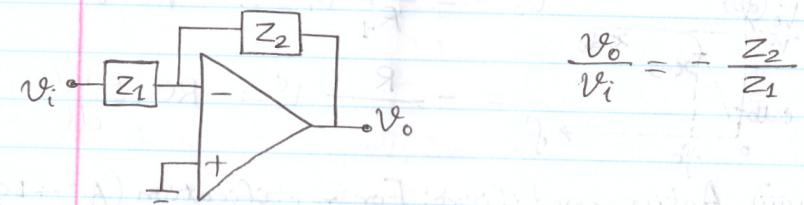vi) Integrator (LPF): Freq. dependent gain




$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1}$$

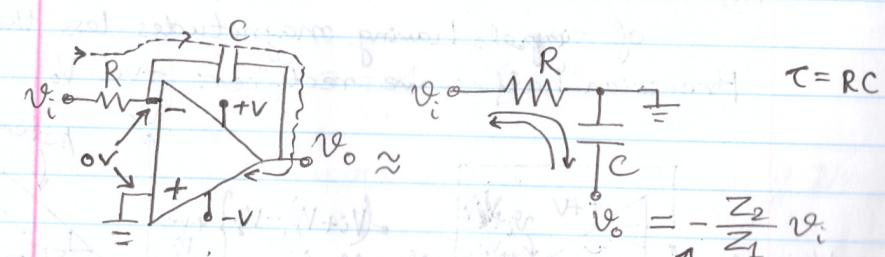

$\tau = RC$   
Phase inversion of 180° is independent of f

$$X_C = \frac{1}{2\pi f C}$$

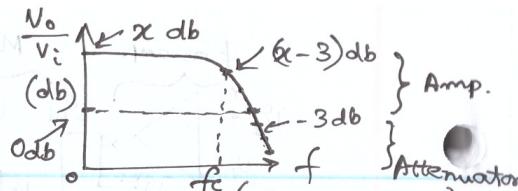

$$V_o = -\frac{1}{SRC} V_i$$


$$\Rightarrow V_o = V_i - \frac{1}{RC} \int_0^t V_i(t) dt \quad (\text{time domain})$$

Initial voltage across 'C' @  $t=0$

If,  $V_c = 0$  at  $t=0$ ;




$$V_o = -\frac{1}{RC} \int_0^t V_i(t) dt$$

vii) Differentiator: HPF

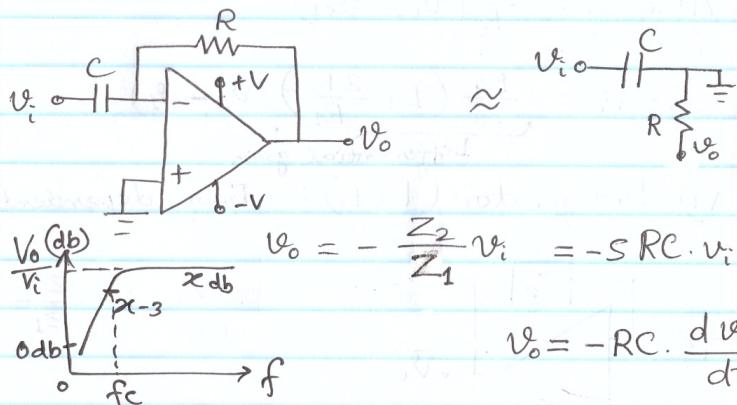


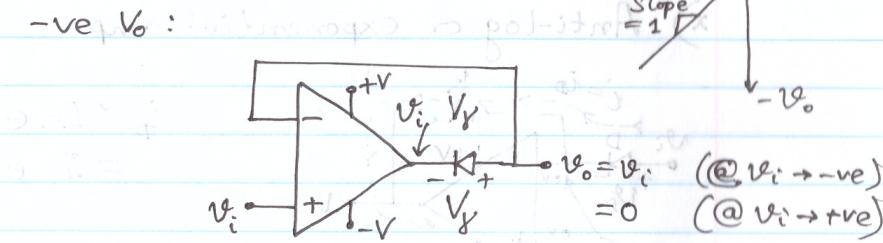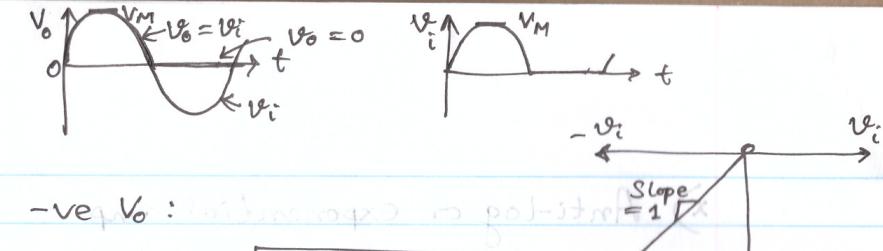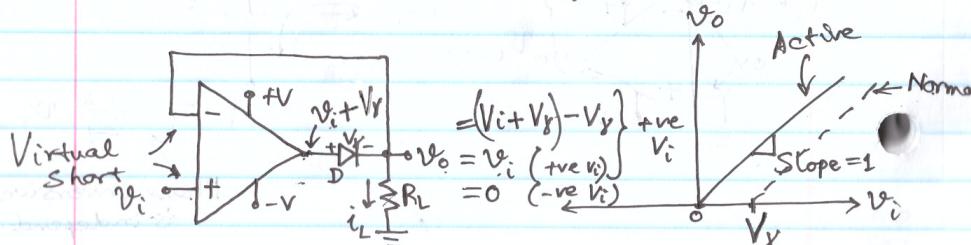viii) Active rectifiers: For rectification ( $AC \rightarrow DC$ ) of signals having magnitudes less than  $V_y$ .

Precision half-wave rectifier: +ve  $V_o$



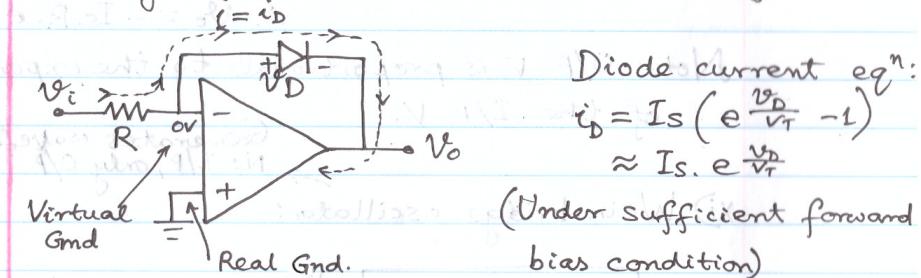ix) Logarithmic amplifier: Natural log computer



$$\text{Diode current eqn: } i_d = I_s (e^{\frac{V_D}{V_T}} - 1)$$

$$\approx I_s \cdot e^{\frac{V_D}{V_T}}$$

(Under sufficient forward bias condition)

$$i_d = I_s \cdot e^{\frac{V_D}{V_T}} = \frac{V_i}{R}$$

$$\Rightarrow I_s \cdot e^{\frac{-V_o}{V_T}} = \frac{V_i}{R} \Rightarrow e^{-\frac{V_o}{V_T}} = \frac{V_i}{I_s \cdot R}$$

Taking natural log on both sides:

$$-\frac{V_o}{V_T} = \ln \left[ \frac{V_i}{I_s \cdot R} \right]$$


$$\Rightarrow V_o = -V_T \cdot \ln \left[ \frac{V_i}{I_s \cdot R} \right]$$

Note: O/P  $V_o$  is proportional to natural log of I/P  $V_i$ .

$$(1 = 18.1) \text{ d}, \text{ with } p = 1$$

add last  
not 2007

x) Anti-log or exponential amp:

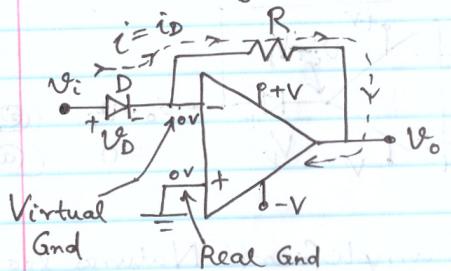


$$i_D \approx I_s e^{\frac{V_o}{V_T}} = I_s e^{\frac{V_i}{V_T}}$$

$$\begin{aligned} V_o &= -i_D \cdot R = -I_s \cdot R e^{\frac{V_i}{V_T}} \\ \Rightarrow V_o &= -I_s \cdot R e^{\frac{V_i}{V_T}} \cdot R \\ \therefore V_o &= -I_s \cdot R^2 e^{\frac{V_i}{V_T}} \end{aligned}$$

Note: O/P V is proportional to the exponent of the I/P V.

Generates waveform  
No I/P, only O/P

x) Wein bridge oscillator:

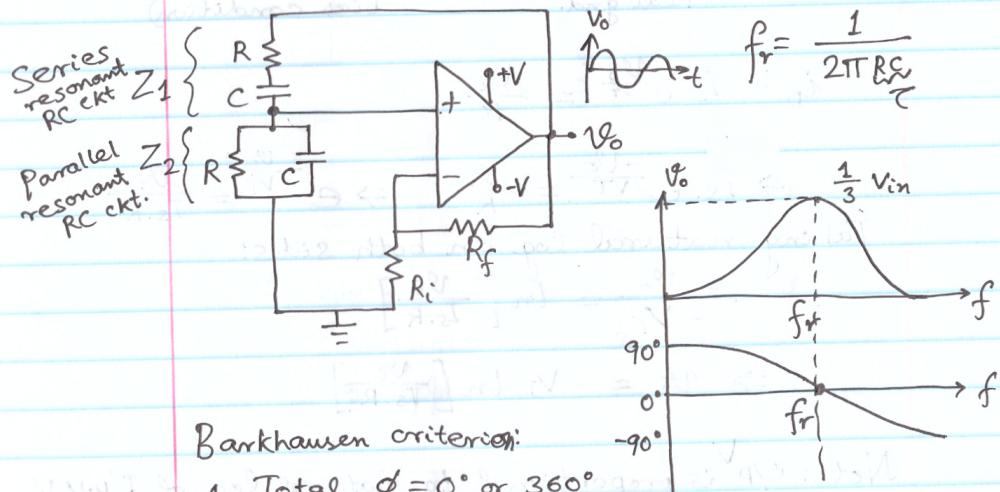


Barkhausen criterion:

1. Total  $\phi = 0^\circ$  or  $360^\circ$
2. +ve f.b. ( $|AB| = 1$ )

$\text{Gain}$        $\text{Feedback factor}$       A combination of +ve f-re f.b.

xii) Comparator: Open-loop V-comparator:

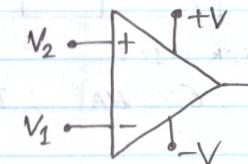

If,  $V_2 > V_1 \Rightarrow V_o = +V_{sat}$   
If,  $V_2 < V_1 \Rightarrow V_o = -V_{sat}$   
(assuming  $A_{od} = \infty$ )