
 

 
## 16. J-K Master-Slave flip-flop:

Clock pulse width is larger than the propagation delay, which causes problem while  $J=K=1$  (toggle mode), as at the end of a clock pulse, O/Ps may/may not toggle to a correct value/logic. Such a problem is solved by using a master-slave FF (Solves the problem of race around)



Clk	$Q_{n-1}$	J	K	$Q_n$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

} Toggle mode is correctly implemented by using J-K M-S FF.

## 17. Logic families: Ckt. & Voltage selection in digital systems.

RTL: Resistor Transistor Logic

DTL: Diode Transistor Logic

TTL: Transistor Transistor Logic

ECL: Emitter Coupled Logic

nMOS & pMOS: n- or p-channel MOS

CMOS: Complementary Metal Oxide Semiconductor

n-MOS logic: Uses only n-ch MOSFETs.

Basic gates:


1) Inverter (NOT)

2) NAND


3) NOR




nMOS NOT Gate:

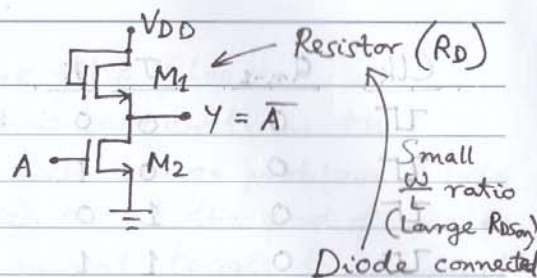

nMOS NAND Gate:

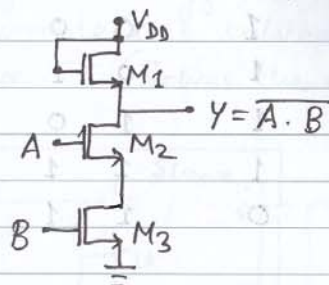


nMOS NOR Gate:

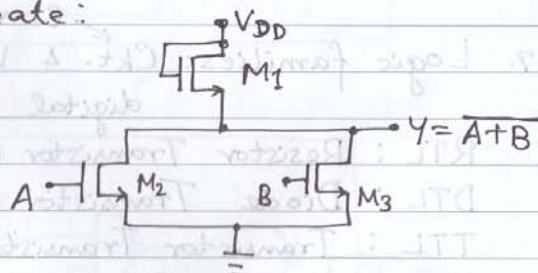

- b) CMOS Logic: Both n-channel & p-channel MOSFETs are used (typically same in number)
- Avoids  $R_D$  or Diode connected MOSFETs.
  - Offers Low power, as current (static) in between  $V_{DD}$  & Gnd is always zero. However (dynamic) current is present during logic transitions only.
  - Smaller area on a Semiconductor integrated circuit (IC).

CMOS NOT Gate

  $A=0, M_1(ON), M_2(OFF), Y=V_{DD}$  $A=1, M_1(OFF), M_2(ON), Y=0V$ 

CMOS NAND Gate:


 $M_1, M_2: PMOS$  $M_3, M_4: NMOS$ 

A	B	Y
0V	0V	$V_{DD}$
0V	$V_{DD}$	$V_{DD}$

$V_{DD}$	0V	$V_{DD}$
$V_{DD}$	$V_{DD}$	0V

CMOS NOR Gate:


A	B	Y
0V	0V	$V_{DD}$
0V	$V_{DD}$	0V
$V_{DD}$	0V	0V
$V_{DD}$	$V_{DD}$	0V

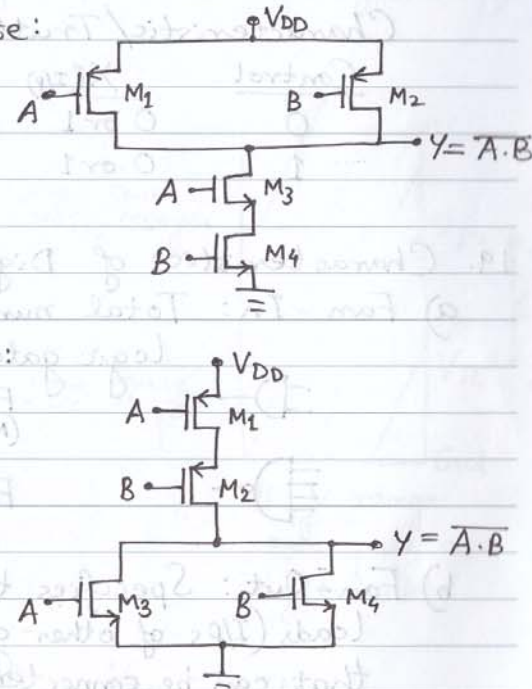


18. CMOS Transmission Gate:

Digitally controlled switch: Analog or Digital  
(Solid-state Semiconductor)  
no moving parts

Signal propagation.

 


Open Switch

 

Closed Switch



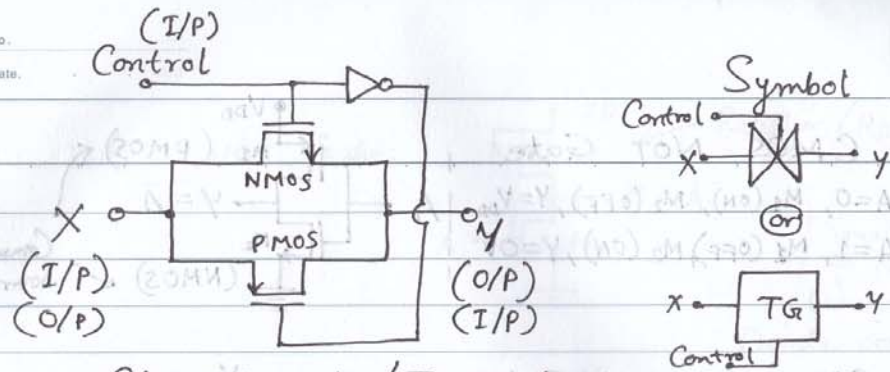


Characteristic/Truth table:


Control	X (I/P)	Y (O/P)
0	0 or 1	Tri-state (or don't care)
1	0 or 1	X (I/P)

## 19. Characteristics of Digital ckt:

 a) Fan-In: Total number of I/Ps in a logic gate. (may be odd or even)




Fan-in = 2  
(No. of I/Ps)

 


Fan-in = 4

 b) Fan-Out: Specifies the number of standard loads (I/Ps of other gates/digital logic I/Ps) that can be connected safely to the O/P of a gate without degrading its normal operation (change in logic state due to excessive loading does not occur)



 
(Same with opp. direction of  $I_{OL}$ , &  $I_{IL}$  if O/P is 0)



$$PD = \frac{t_r + t_f}{2}$$

c) Propagation delay: Average transition delay time for signal to propagate from an I/P to its O/P when a binary I/P signal changes a value/logic.  
(Time delay of a gate or any digital ckt)

d) Noise margin:

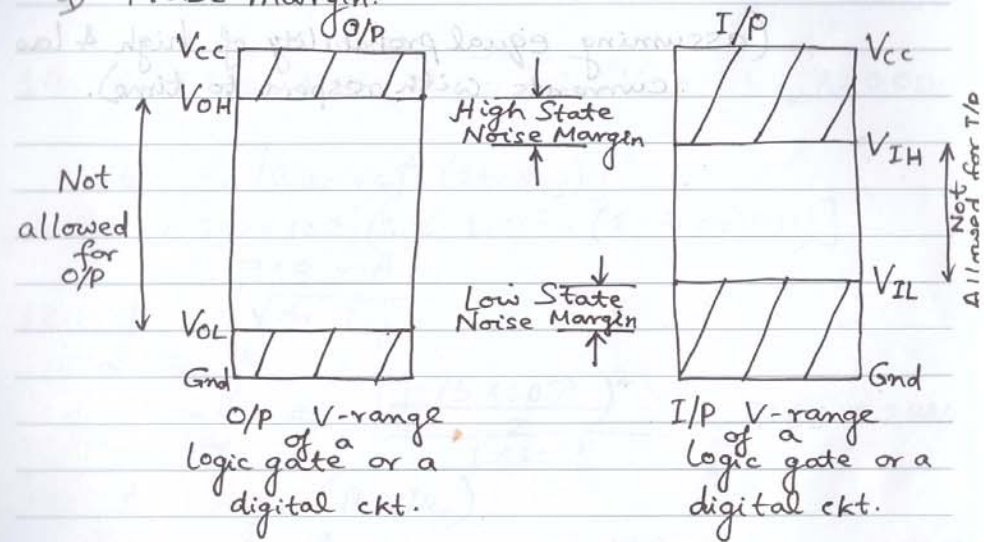

$$\text{Noise margin (high)} = V_{OH} - V_{IH}$$

$$\text{Noise margin (low)} = V_{IL} - V_{OL}$$

where,

$V_{OH}$ : Voltage O/P high ('1' state)

$V_{OL}$ : " " low ('0' state)

$V_{IH}$ : " I/P high ('1' state)

$V_{IL}$ : " " low ('0' state)